

93743

11111111111111111111

M-533

Sl. No.

Total No. of Pages : 3

**III Semester B.Sc. Examination, March/April - 2021
(Semester Scheme) (CBCS)
PHYSICS**

Electricity and Electromagnetism (Paper - III)

Time : 3 Hours

Max. Marks : 80

Instruction : Answer any Two from PART-A, any Two from PART-B, any Three from PART-C and any Ten from PART-D.

PART - A

1. a) Give the thermodynamic theory of thermoelectric effect. [7]
b) State and prove Thevenin's theorem. [5]
2. a) Derive wave equation for the field vectors in free space. [6]
b) Describe Hertz experiment for the production and detection of electromagnetic waves. [6]
3. a) Set up the Maxwell's field equations. [6]
i) $\vec{\nabla} \cdot \vec{E} = \rho / \epsilon_0$
ii) $\vec{\nabla} \times \vec{E} = -\frac{\partial \vec{B}}{\partial t}$
b) State and explain Stoke's theorem. [3]
c) Explain the physical significance of divergence of a vector field. [3]

PART - B

4. a) Explain the growth of current in series RLC circuit and arrive at an expression for current in it. [6]
b) State and prove maximum power transfer theorem. [6]

P.T.O.


93743

M-533

5. a) Obtain an expression for instantaneous current in an RL circuit fed with an AC, also give the expression for phase angle between current and voltage. [5]
- b) Derive an expression for self inductance of a coil using Anderson's bridge. [7]
6. a) What is high pass filter? Discuss the frequency response of high pass RC filter and obtain an expression for cut-off frequency. [6]
- b) Give the construction and working of CRO. [6]

PART - C

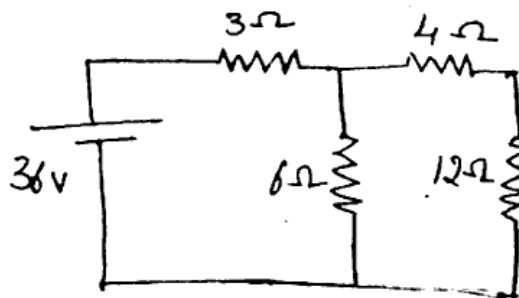7. Calculate the thermo emf of silver Iron thermo couple with the junctions at 0° and 90°C given $a = 13.31 \mu\text{V}/^\circ\text{C}$ and $b = -0.019 \mu\text{V}/^\circ\text{C}$. Calculate its neutral temperature. [4]
8. A circuit having capacitor of capacitance $10 \mu\text{F}$ in series with a resistance of 5Ω is fed to 200 V , 50 Hz ac supply calculate the maximum current and power factor. [4]
9. Using Norton's theorem calculate the current flowing through 12Ω resistor shown in circuit diagram. [4]



10. A coil of self inductance 10 H in series with a resistance of 100Ω is connected to a 100V dc supply. Calculate the time constant of the circuit. What is the final steady state value of current? [4]

<https://www.uomonline.com>

<https://www.uomonline.com>

743

M-533

PART - D

- a) Explain seebeck effect. [2]
- b) State superposition theorem. [2]
- c) State Kirchhoff's voltage law. [2]
- d) What is intrinsic impedance of free space? Explain. [2]
- e) What is Displacement Current? Explain. [2]
- f) Explain the concept of oscillating dipoles. [2]
- g) Define Quality factor of a series resonant circuit. [2]
- h) What is power factor in a AC circuit? Explain. [2]
- i) Define root mean square value of AC. [2]
- j) What are Band pass filters? Explain. [2]
- k) Define Half-power frequencies of a series LCR circuit fed with AC. [2]
- l) Draw the circuit diagram of De sauty bridge and hence give the condition for balance. [2]

